

# \* Digital Electronics and Logic Design (DELD) - Practical Number - 23

Name:- Haustush Shrikant Kabra

Class:- Second Year Engineering

Div:- A Roll Number:-

Batch:-

Department:- Computer Engineering Department

College:- AISSMS's IOT T.

Title:-

Design and Implement code converters  
a) Binary to Gray  
b) BCD to Excess-3.

Aim:-

To Design and understand the code converters:-  
a) Binary to Gray  
b) BCD to Excess-3

Theory:-

a) Binary Number-

A number represented by the digits '0' and '1' is called binary number. Example:-

- i) 001
- ii) 100
- iii) 011

b) Gray Code-

In gray code, bit patterns for two consecutive numbers differ in only one bit position. Its application is it is use in which the normal sequence of binary number generated by the hardware may produce an error during transition from one number to another.

Example:-  
Binary 011 → Gray 010




### c) Binary Coded Decimal Number (BCD) -

BCD is a class of encoding of a decimal number where each digit is represented by a fixed number of bits, usually four or eight. Four bit BCD can represent 16 numbers i.e. from 0(0000) to 15(1111).


### d) Excess-3 $\rightarrow$

It is a non-weighted code used to express code to express a decimal number. It is particularly significant for arithmetic operations as it overcomes shortcomings encountered.
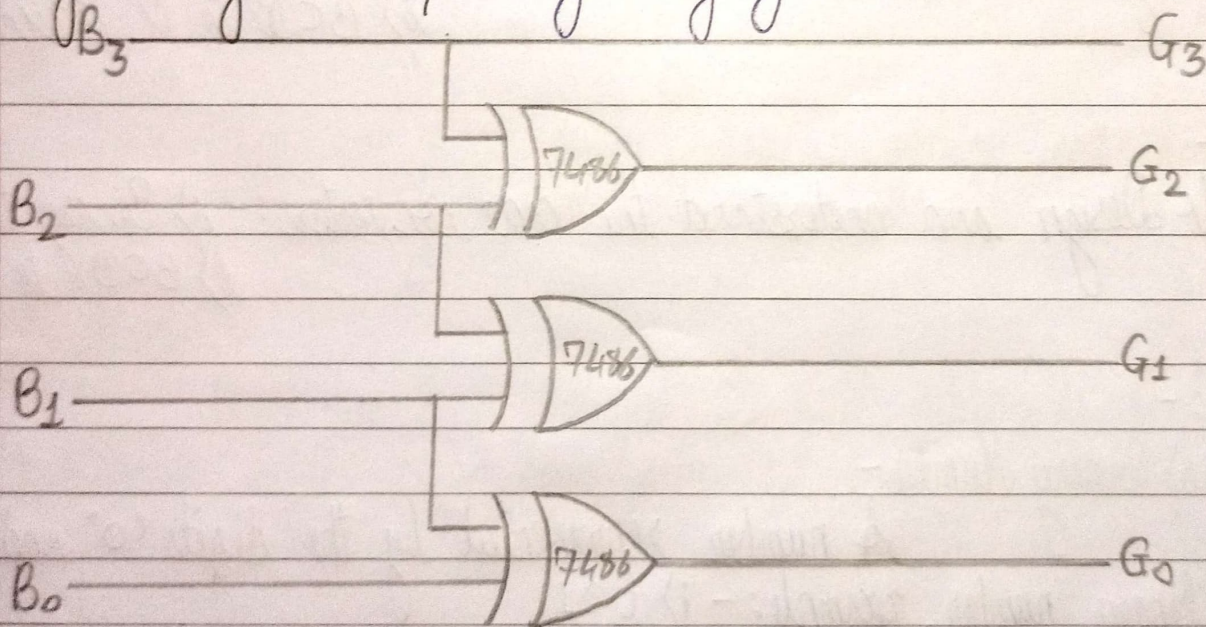
### Logic Diagram: $\rightarrow$ a) Binary to Gray: -




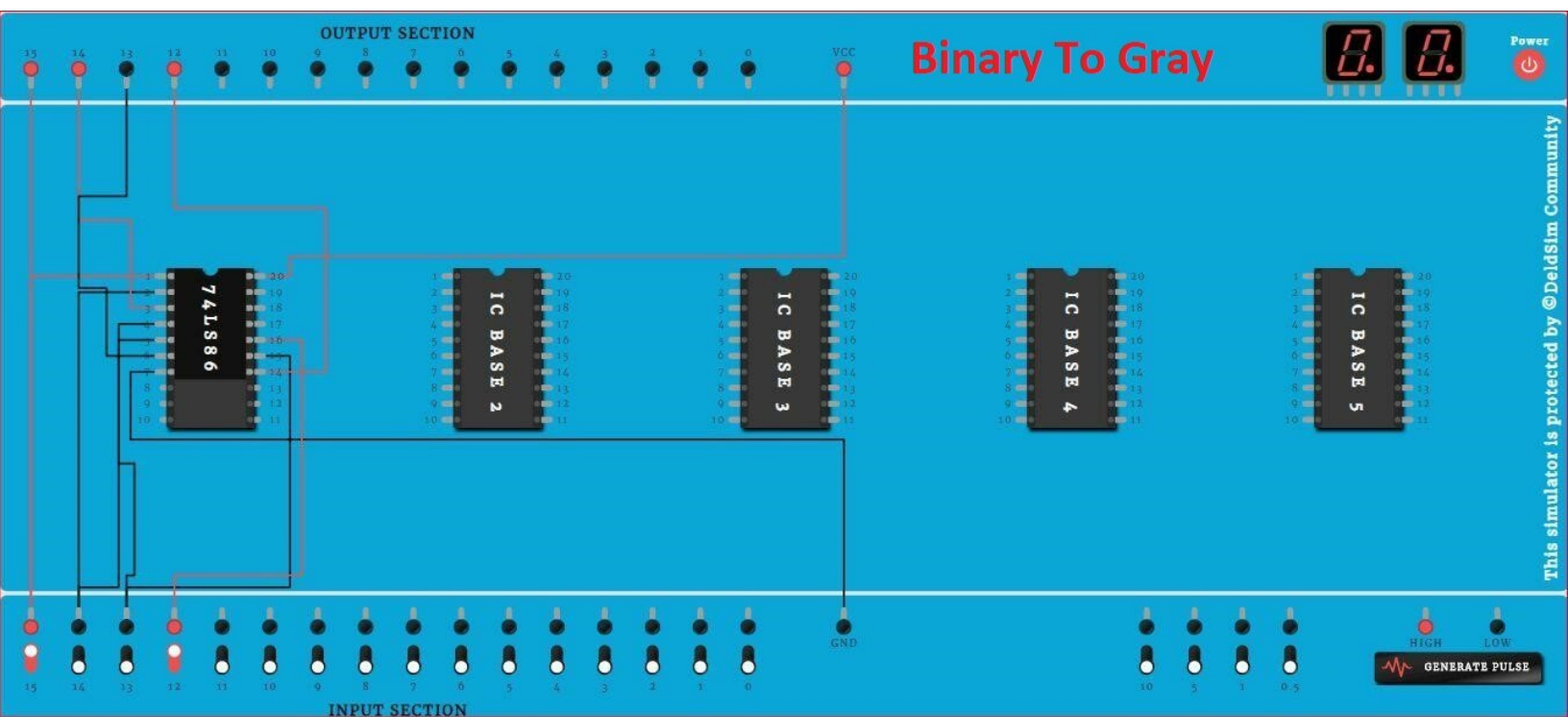IC 7486  $\rightarrow$  2-Input XOR gate.






b) BCD to Excess 3:-

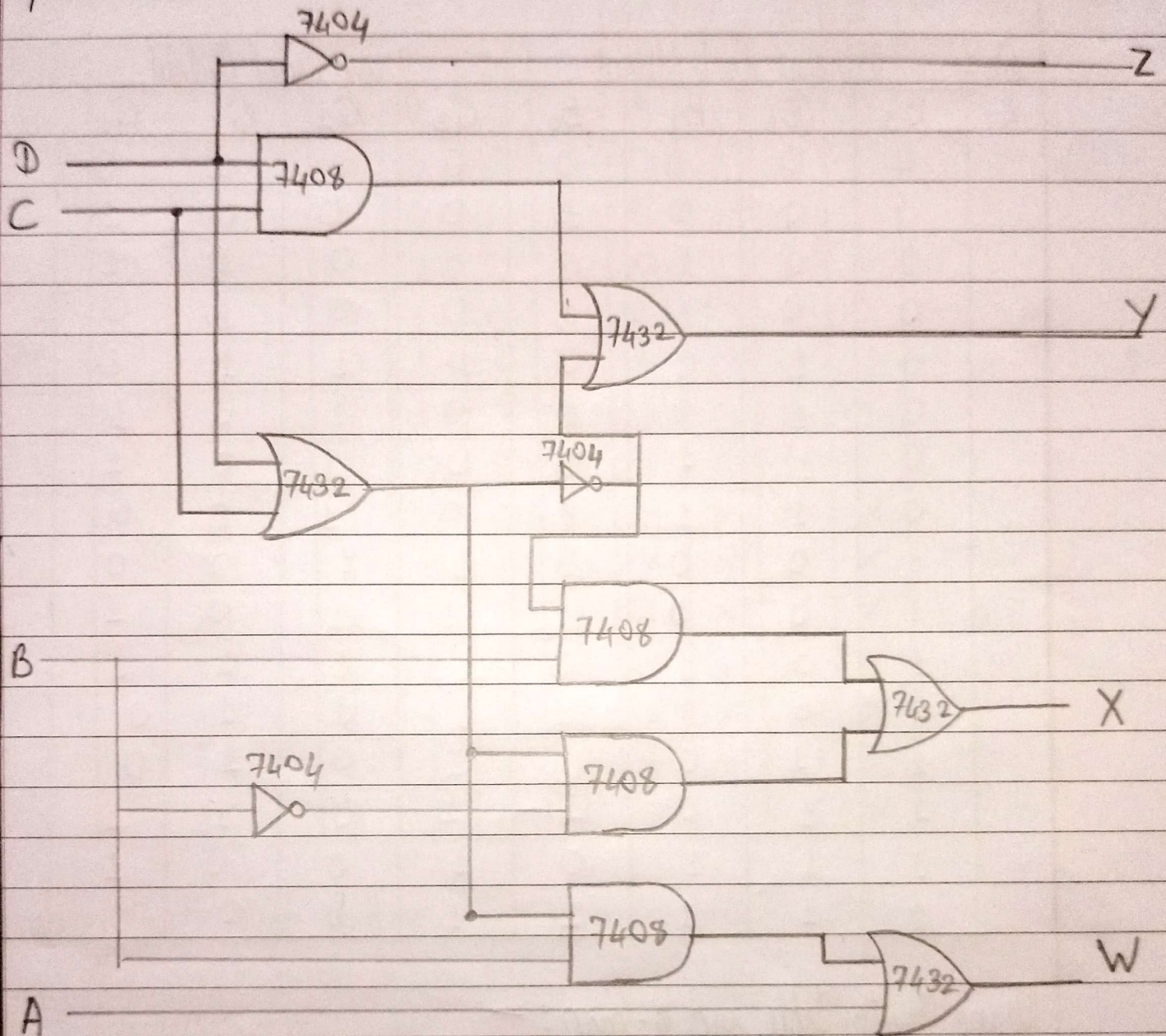

IC 7404 → NOT gate.

IC 7408 → 2-Input AND gate

IC 7432 → 2-Input OR gate.

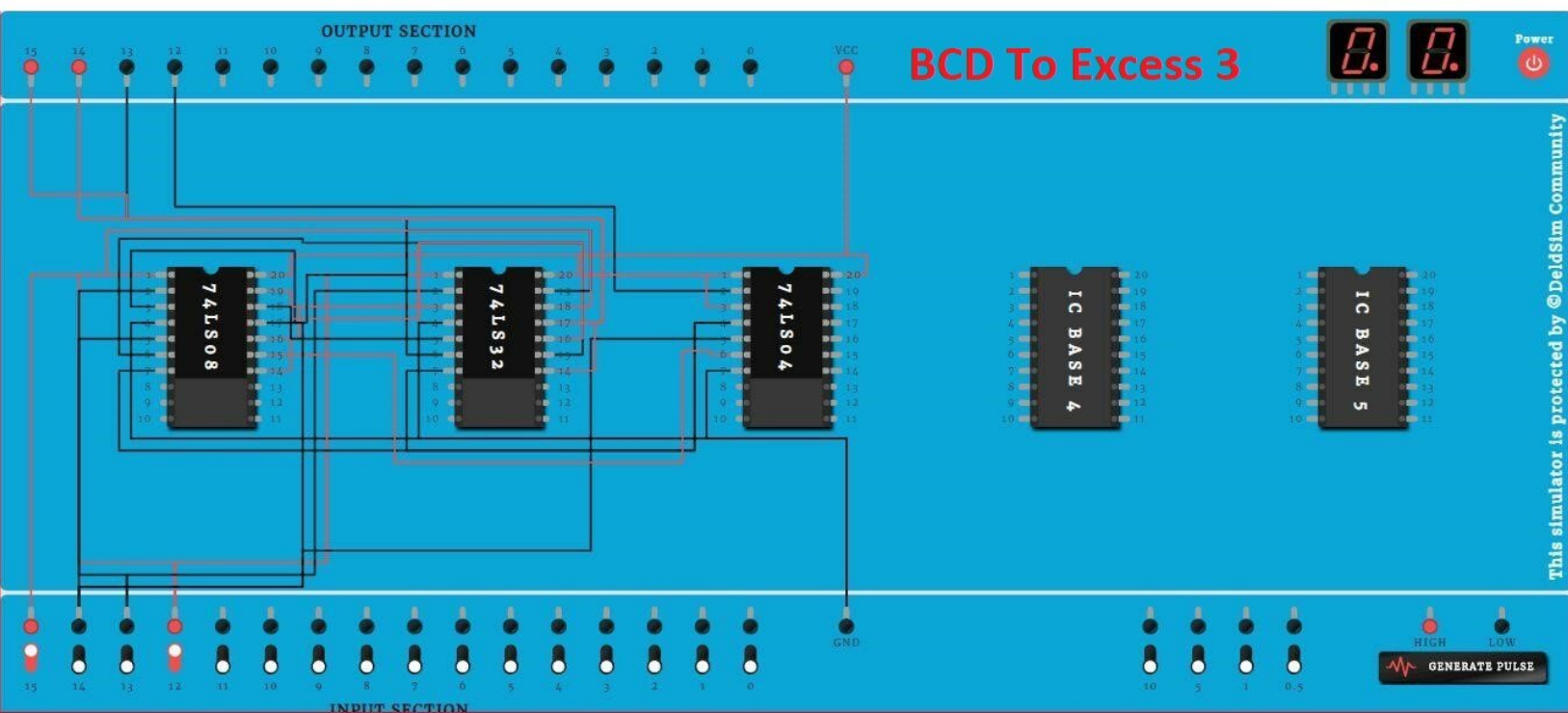



Truth Table: -

a) →	Binary Code/ Input				Gray Code/ Output			
	$B_3$	$B_2$	$B_1$	$B_0$	$G_3$	$G_2$	$G_1$	$G_0$
	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	1
	0	0	1	0	0	0	1	1
	0	0	1	1	0	0	1	0
	0	1	0	0	0	1	1	0
	0	1	0	1	0	1	1	1
	0	1	1	0	0	1	0	1
	0	1	1	1	0	1	0	0
	1	0	0	0	1	1	0	0
	1	0	0	1	1	1	0	1
	1	0	1	0	1	1	1	1
	1	0	1	1	1	1	1	0
	1	1	0	0	1	0	1	0
	1	1	0	1	1	0	1	1
	1	1	1	0	1	0	0	1
	1	1	1	1	1	0	0	0

Using Truth Table and K-map: -

$$G_3 = B_3$$

$$G_2 = B_2 \oplus B_3 / B_2 \text{ XOR } B_3$$

$$G_1 = B_1 \oplus B_2 / B_1 \text{ XOR } B_2$$

$$G_0 = B_0 \oplus B_1 / B_0 \text{ XOR } B_1$$



b) →	Decimal	BCD				Excess-3			
		A	B	C	D	W	X	Y	Z
	0	0	0	0	0	0	0	1	1
	1	0	0	0	1	0	1	0	0
	2	0	0	1	0	0	1	0	1
	3	0	0	1	1	0	1	1	0
	4	0	1	0	0	0	1	1	1
	5	0	1	0	1	1	0	0	0
	6	0	1	1	0	1	0	0	1
	7	0	1	1	1	1	0	1	0
	8	1	0	0	0	1	0	1	1
	9	1	0	0	1	x	x	x	x
	10	1	0	1	0	x	x	x	x
	11	1	0	1	1	x	x	x	x
	12	1	1	0	0	x	x	x	x
	13	1	1	0	1	x	x	x	x
	14	1	1	1	0	x	x	x	x
	15	1	1	1	1	x	x	x	x

Using Truth table and K-map: -

$$W = A + BC + BD$$

$$X = B'C + B'D + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$



Outcome:-

From the experiment we learnt to design and analyze binary to Gray and BCD to Excess-3 code converter.

Conclusion:-

Hence, we have designed and implemented binary to gray and 1) BCD to Excess-3.