

* Digital Electronics and Logic Design (DELD) - Practical Number - 2

Name:- Kaustubh Shrikant Habra

Class:- Second Year Engineering

Div:- A

Roll Number:-

Batch:-

Department:- Computer Engineering Department

College:- AISSMS, IOIT.

Title:-

Full Adder and Full Subtractor

Aim:-

To realize full adder and full subtractor using

a) Basic Gates

b) Universal Gates.

Objective:-

Understanding the working of full adder and full subtractor by
only using a) Basic Gates
b) Universal Gates.

Theory:-

a) Full Adder:-

The half adder does not take the carry bit from its previous stage into account. This carry bit from its previous stage is called carry-in bit. A combinational logic circuit that adds two data bits, x_1 and x_2 and a carry-in bit, C_{in} , is called a full

sdder. The Boolean functions describing the full-adder are:

$$S = (x \oplus y) \oplus C_{in}$$

$$C = xy + C_{in}(x \oplus y)$$

b) Full Subtractor:-


Subtracting two single-bit binary values, B, C_{in} from a single-bit value A produces a difference bit D and a borrow out B_r bit. This is called full subtraction. The boolean functions describing the full-subtractor are:

$$D = (A \oplus B) \oplus C_{in}$$

$$B_r = A'B + A'(C_{in}) + B(C_{in})$$


Logic Diagram:-

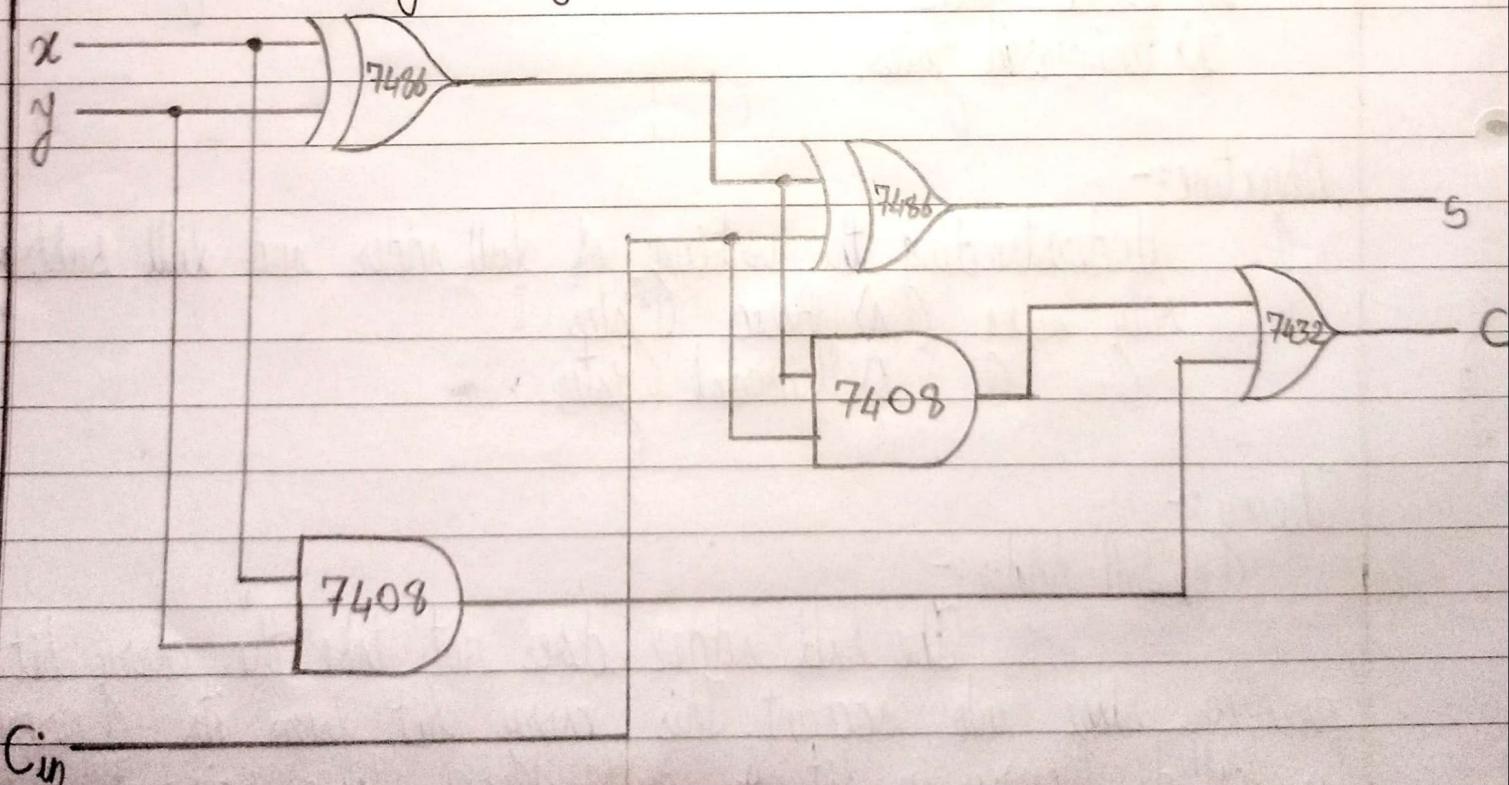a) Full Adder Using Basic Gates \rightarrow




IC 7486 \rightarrow 2-Input XOR gate, IC 7408 \rightarrow 2-Input AND gate


IC 7432 \rightarrow 2-Input OR gate.

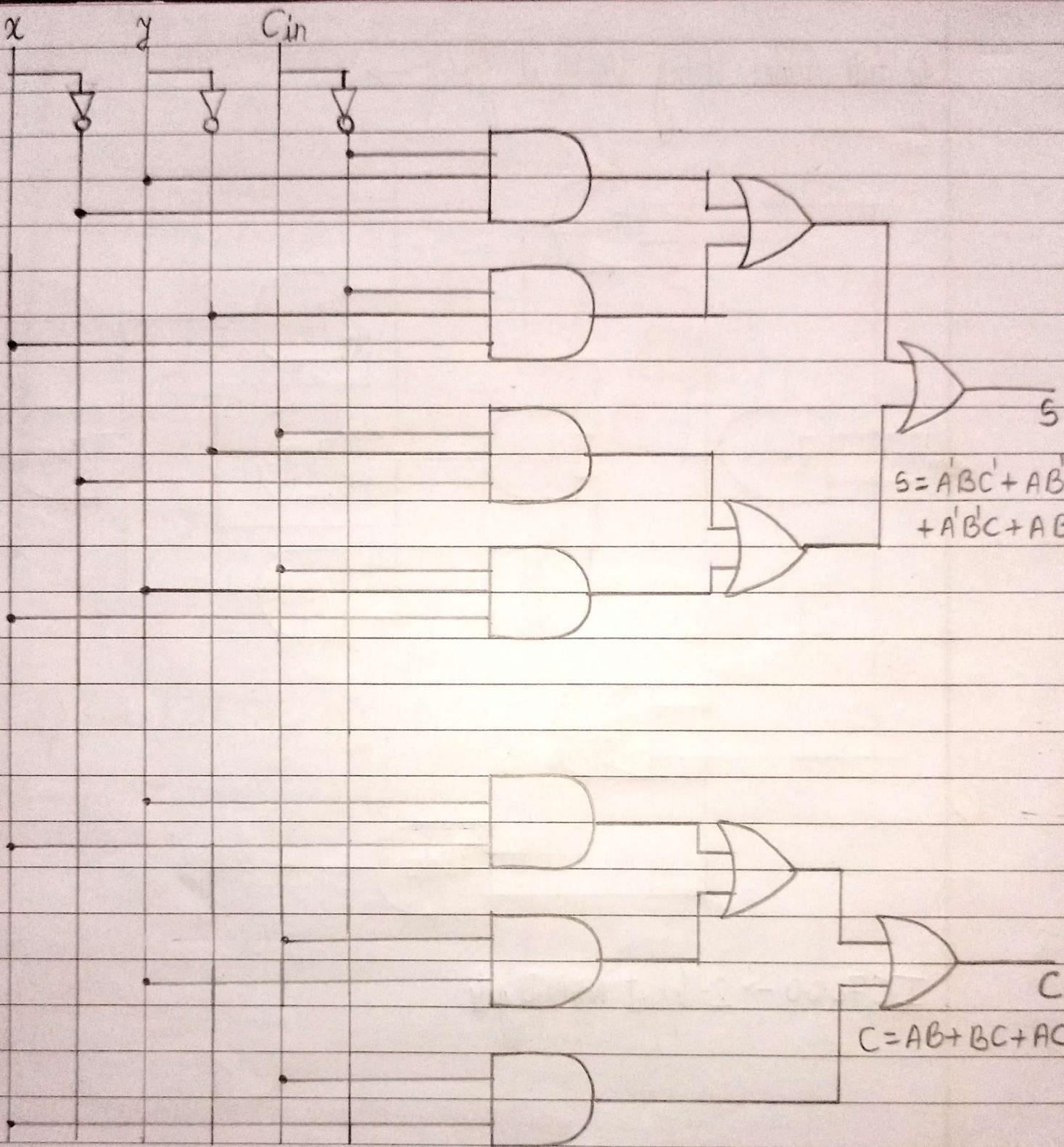


Full Adder Using Basic Gates

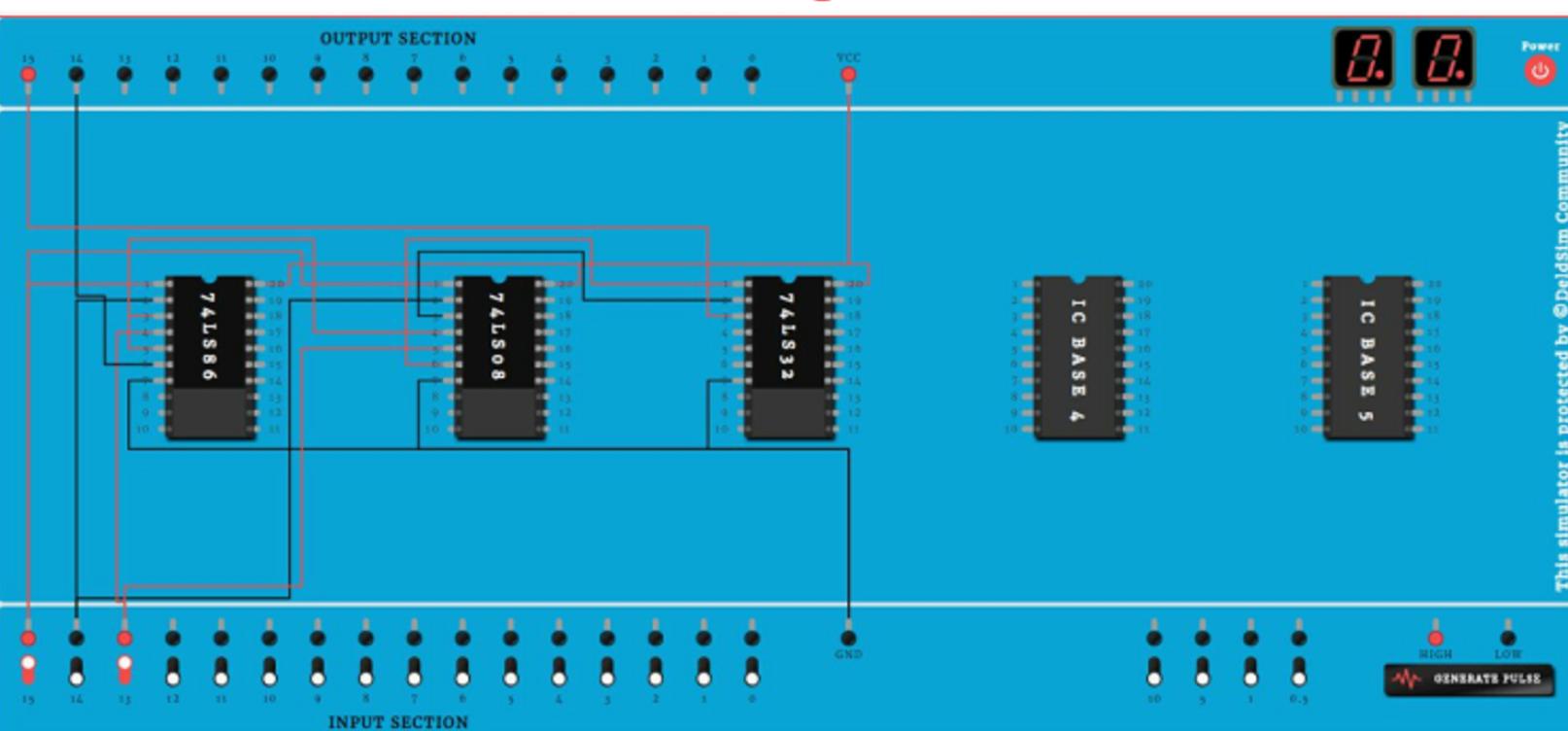

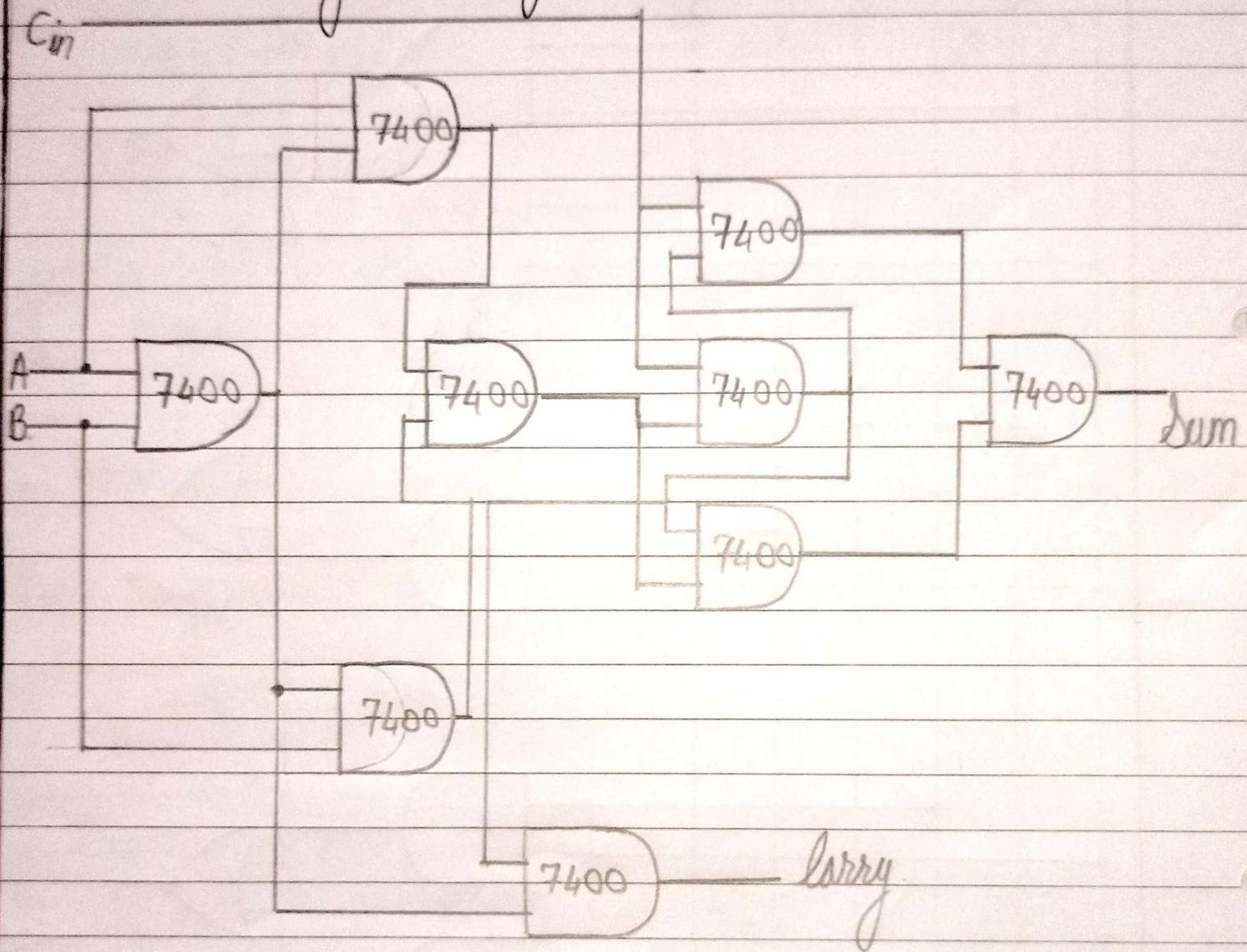
b) Full Adder Using Universal Gates \rightarrow



IC 7400 → 2-Input NAND gate.

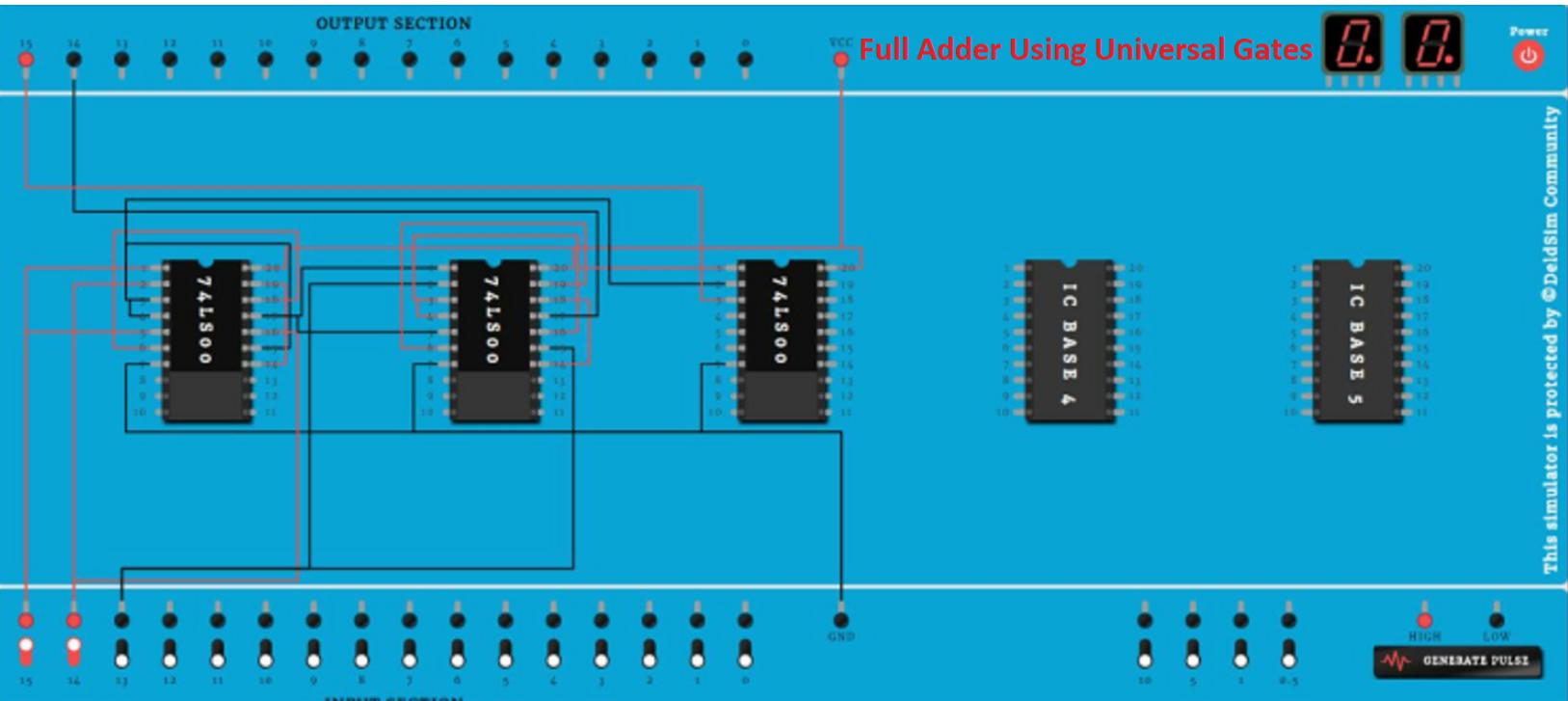


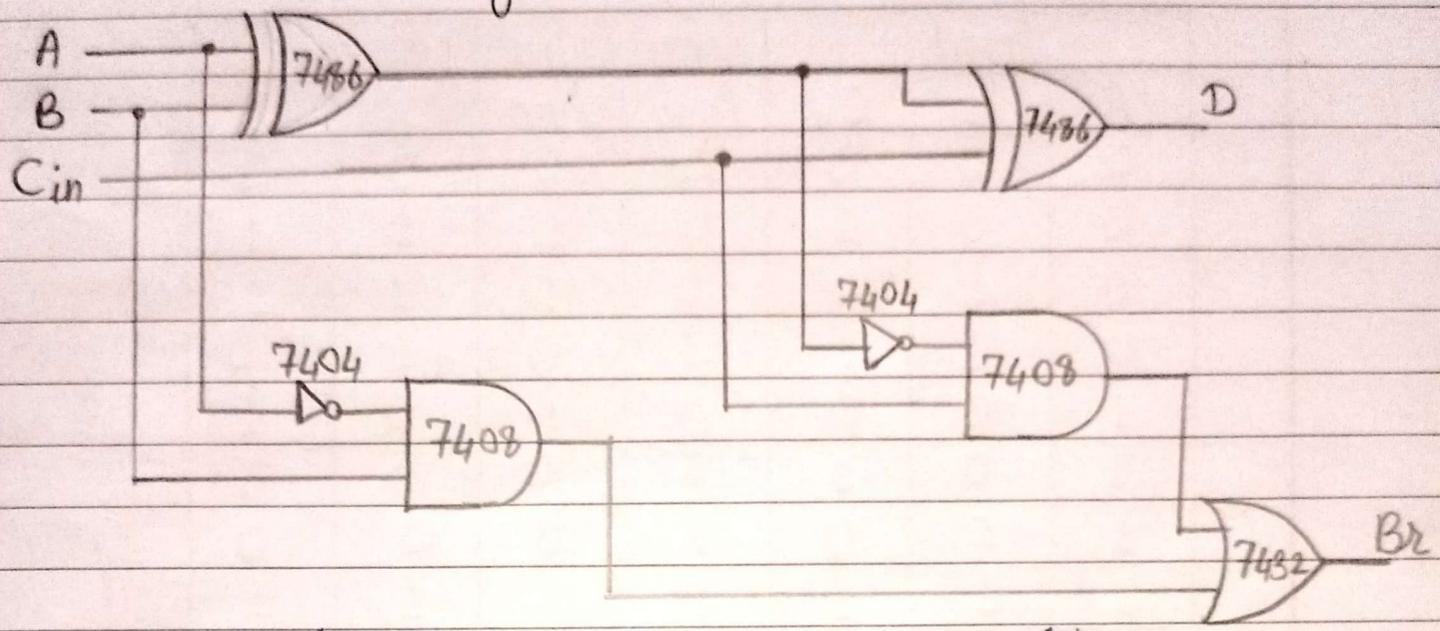c) Full Subtractor Using Basic Gates \rightarrow



IC 7486 \rightarrow 2 Input XOR gate, IC 7404 \rightarrow NOT gate
IC 7408 \rightarrow 2-Input AND gate, IC 7432 \rightarrow 2-Input OR gate.

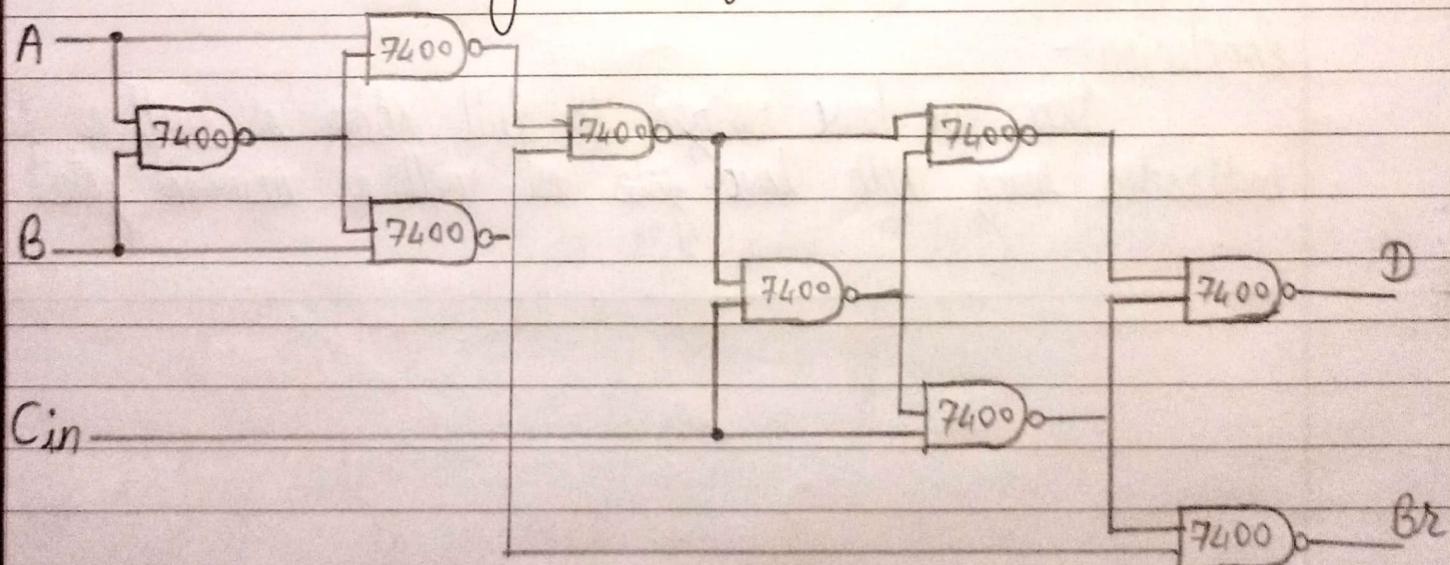d) Full Subtractor Using Universal Gates \rightarrow




IC 7400 \rightarrow 2-Input NAND gate.

Power



This simulator is protected by © DeisSim Community

Full Subtractor Using Basic Gates

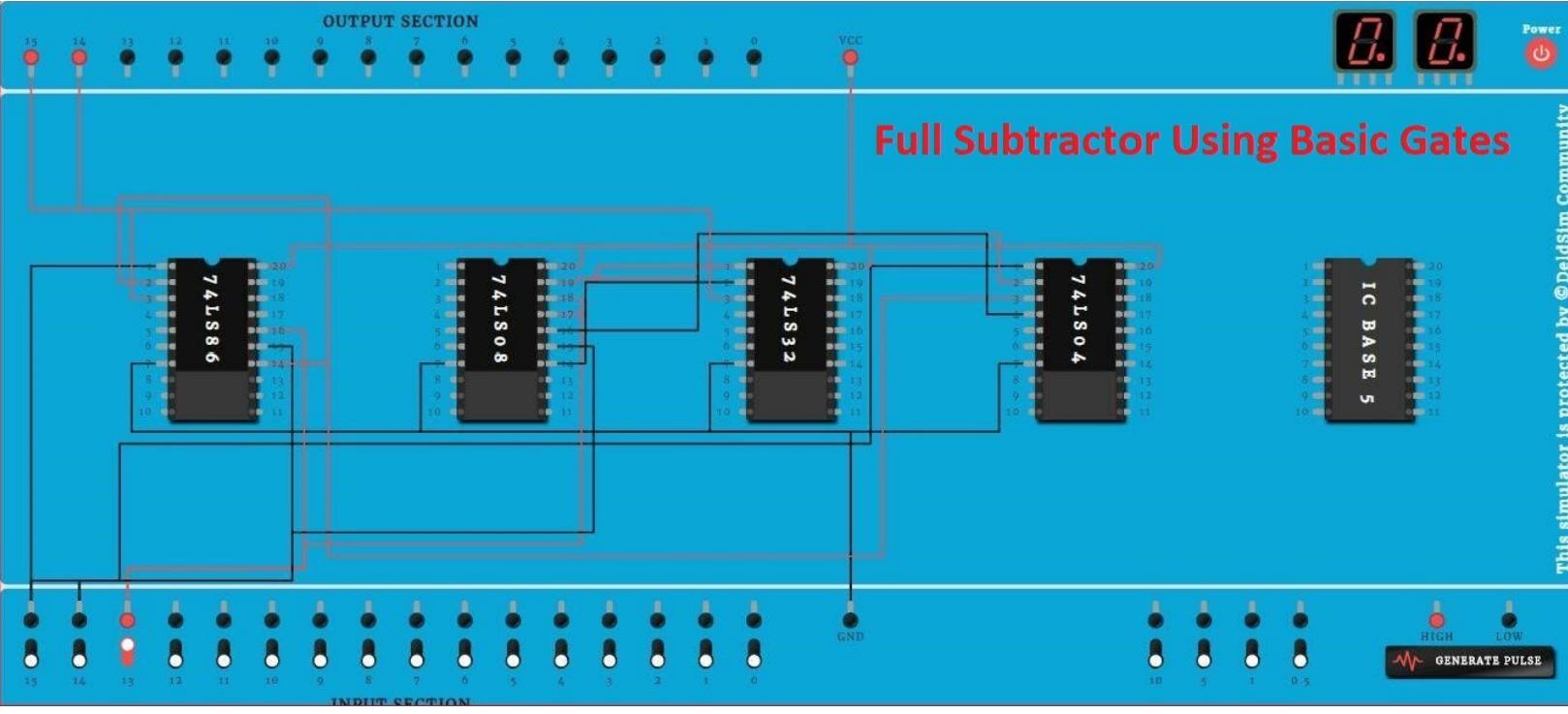


Power



This simulator is protected by © DeisSim Community

Full Subtractor Using Universal Gates

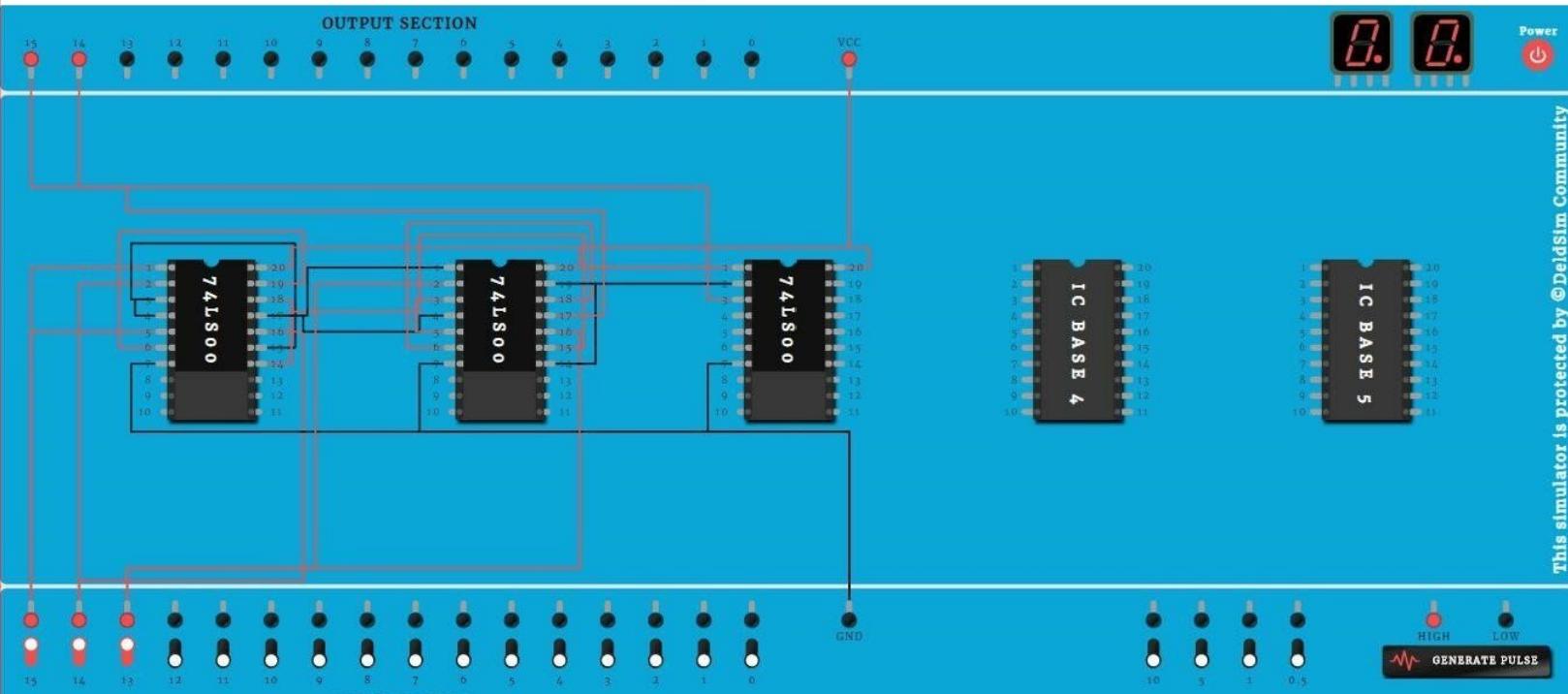

Truth Table :-

Input			Adder Output		Subtractor Output	
A	B	Cin	Carry	Sum	Br	D
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	1	0	0	0
1	1	0	1	0	0	0
1	1	1	1	1	1	1

Outcomes :-

Thus we have learned how to design and how it works using both basic gates and universal gates.

Conclusion :-

Hence we have realized the full adder as well as full subtractor using both basic gates as well as universal gates.